


Field Programmable Gate Arrays

FPGA


Using ROM as Combinational Logic

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

tt1

 

schem1



 


F

lut1

Mapping Larger Functions To ROMs

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

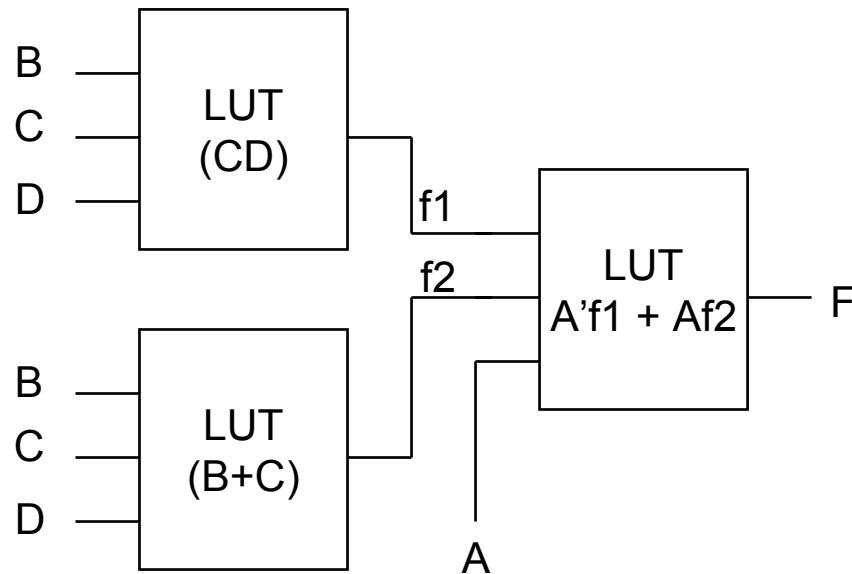  


Very similar to how we decomposed functions to implement with MUX blocks...


ROM vs. LUT

- A ROM can be used as a lookup table (LUT)
- An FPGA contains many, many such LUTs
 - 1,000's of them
- A 3LUT has 3 inputs + 1 output
- A 4LUT has 4 inputs + 1 output
- 3LUTs and 4LUTs are most common...


Mapping a Gate Network to LUTs

 

Mapping a Gate Network to 3LUTs

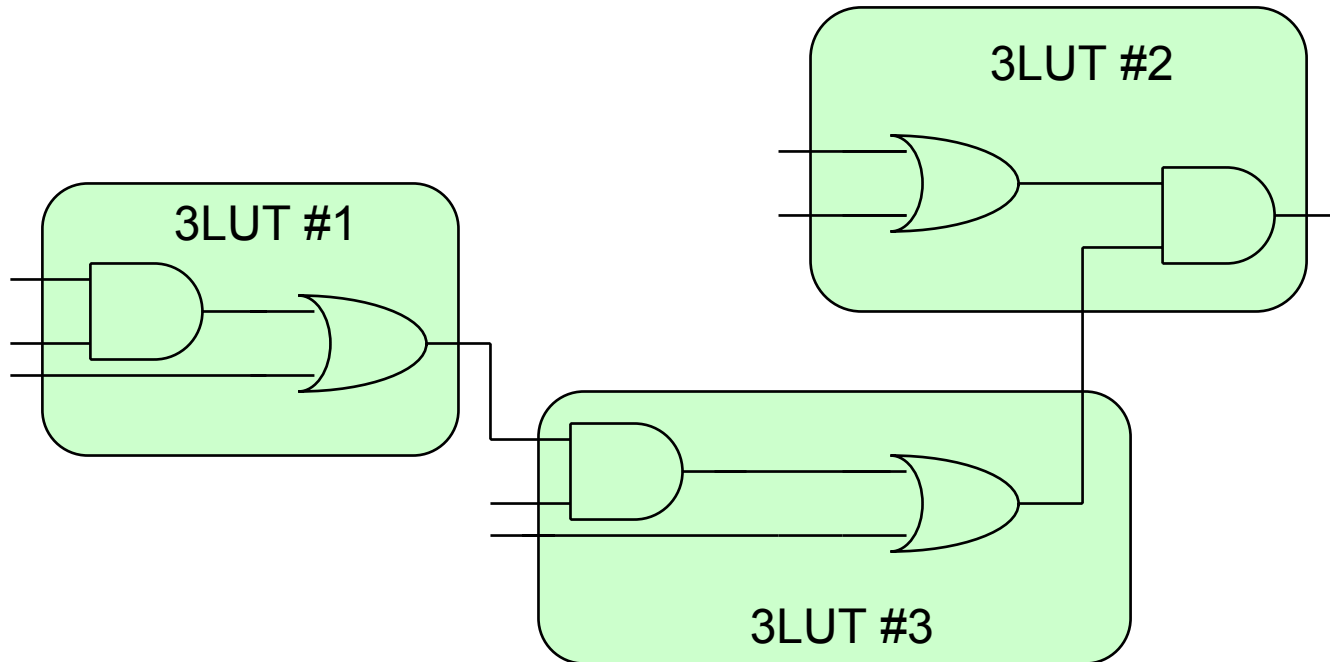

Mapping Same Network to 4LUTs

 

Mapping Equations to LUTs

- Each of these equations require 1 LUT:

$$F = a$$

$$F = abcd$$

$$F = a'b'c'd + a'bcd' + a'b'c'd' + a'b'cd$$

$$F = a + b + c + d$$

$$F = (a + b + c + d)(a' + b' + c' + d')$$


Not a function of equation complexity,
is a function of # unique inputs

FPGAs - What Are They?

Programmable logic elements
(LEs)

Programmable wiring areas

 
I/O Buffers communicate
between FPGA and
the outside world



An FPGA is a Programmable Logic Device (PLD)
It can be programmed to perform any function desired.


Programmable Logic Elements (LEs)

 - Typically contain a LUT, wires, and storage



Programmable Logic Elements (LEs)

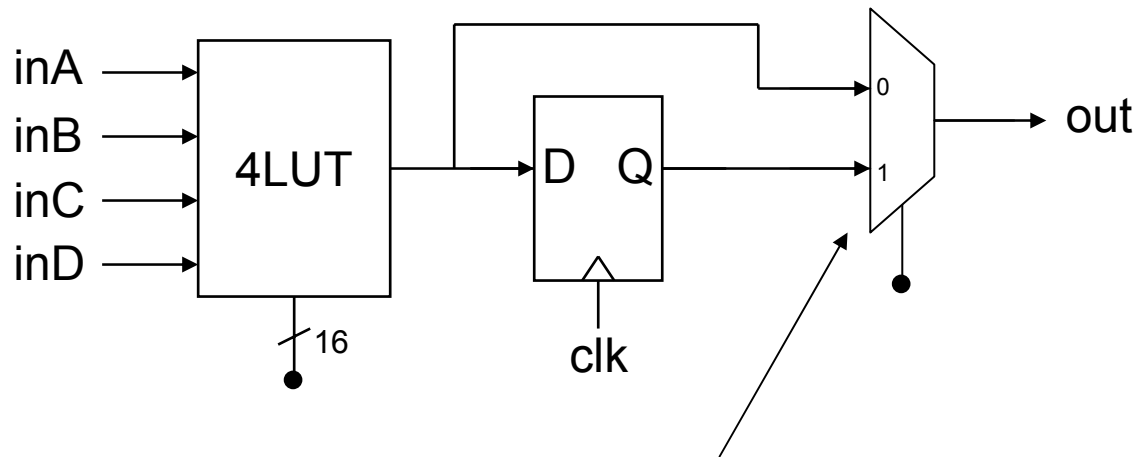
- Typically contain a LUT, wires, and storage



This one provides a registered or unregistered function of the 4 input variables

Programmable Logic Elements (LEs)

 
- Typically contain a LUT, wires, and storage



Black dots indicate programming bits
(configuration bits)

Programmable Logic Elements (LEs)

 
- Typically contain a LUT, wires, and storage



On power up, configuration bits are loaded into FPGA
This customizes its operation (LUT function, MUX selection)

Programmable Logic Elements (LEs)

 
- Typically contain a LUT, wires, and storage




Typically, configuration bits are not changed during circuit operation
(but, some FPGA's are *dynamically reconfigurable*)

Another LE Structure

 
- Provides two outputs
 - One combinational, one registered




One Configuration

 


Another Configuration

 

Yet Another Configuration

 

An LE With Carry/Cascade Logic

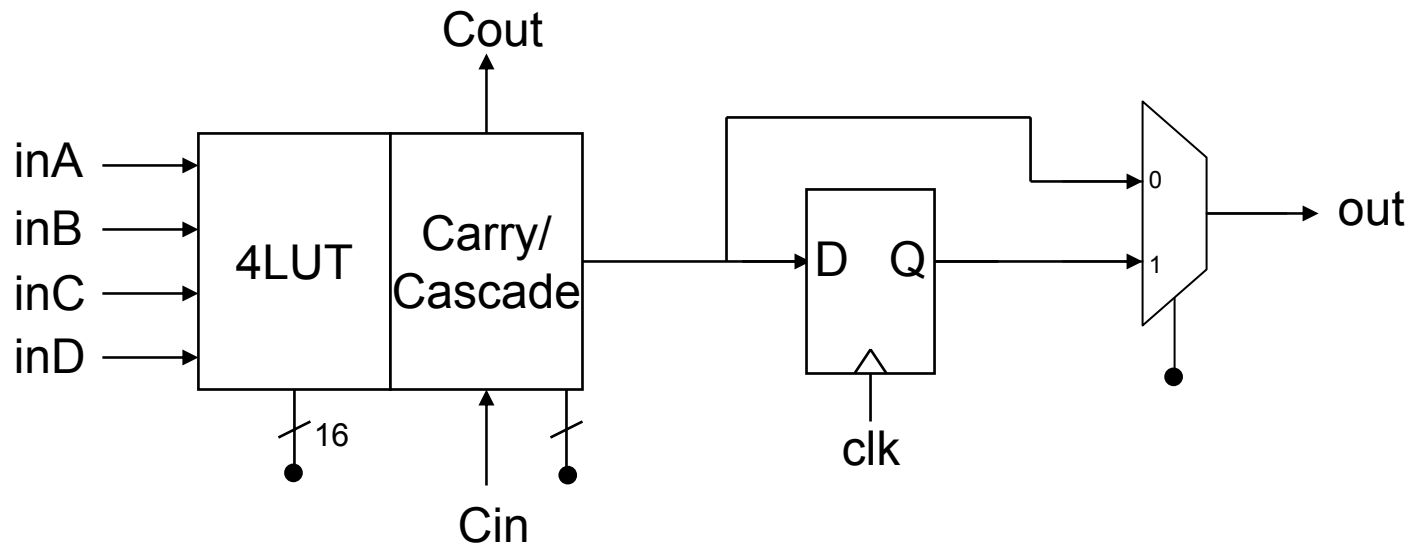


Can do two functions at once (cout and Cout)

Carry/cascade logic optimized for add/subtract + wide AND,OR, ...

Cin and Cout have dedicated connections to neighboring LEs ⇔ fast carry chains ⇔ fast arithmetic




An FPGA Architecture (Island Style)

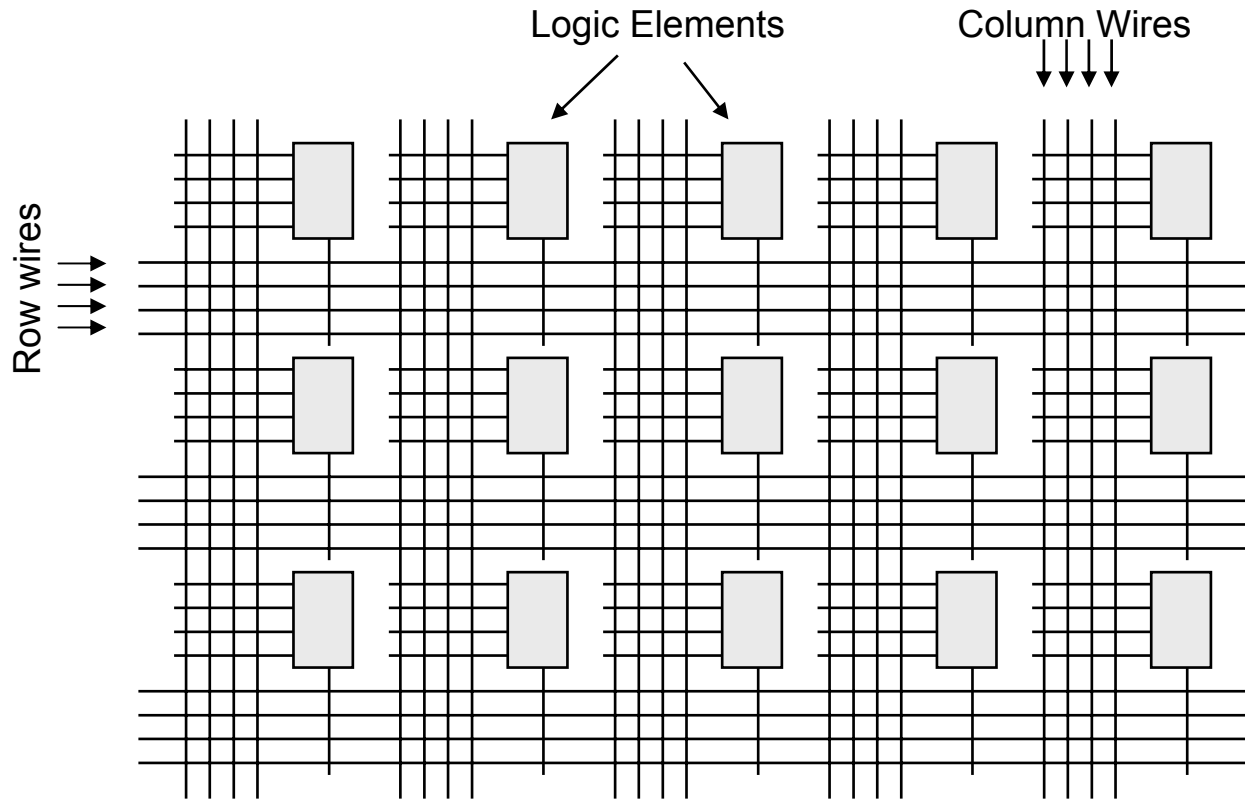

Each LE is configured to do a function




Wire intersections are programmed to either connect or not

Programmable Interconnect Junction

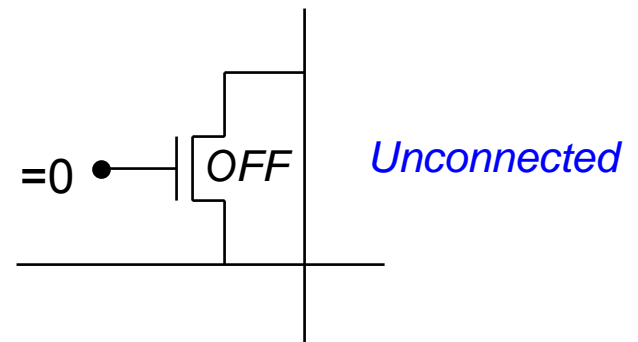 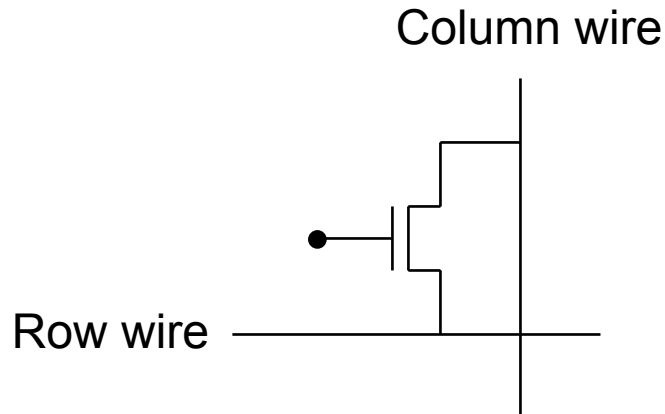

   
Example Problem

- Generate the N, Z, P status flags for a microprocessor




 Example Problem


- Generate the N, Z, P status flags for a microprocessor




Will require 2 4LUTs

 

 Can be done with wiring only or with 1 4LUT



Will require 1 4LUT

 


LUT #1: $F1 = D0' \cdot D1' \cdot D2' \cdot D3'$

LUT #7: $F2 = F1 \cdot D4' \cdot D5' \Leftrightarrow Z$ output

LUT #8: $F3 = D5 \Leftrightarrow N$ output

 LUT #9: $F4 = Z' \cdot N' \Leftrightarrow P$ output




LUT #1: $F1 = D0' \cdot D1' \cdot D2' \cdot D3'$

LUT #7: $F2 = F1 \cdot D4' \cdot D5' \Leftrightarrow Z$ output

LUT #8: $F3 = D5 \Leftrightarrow N$ output

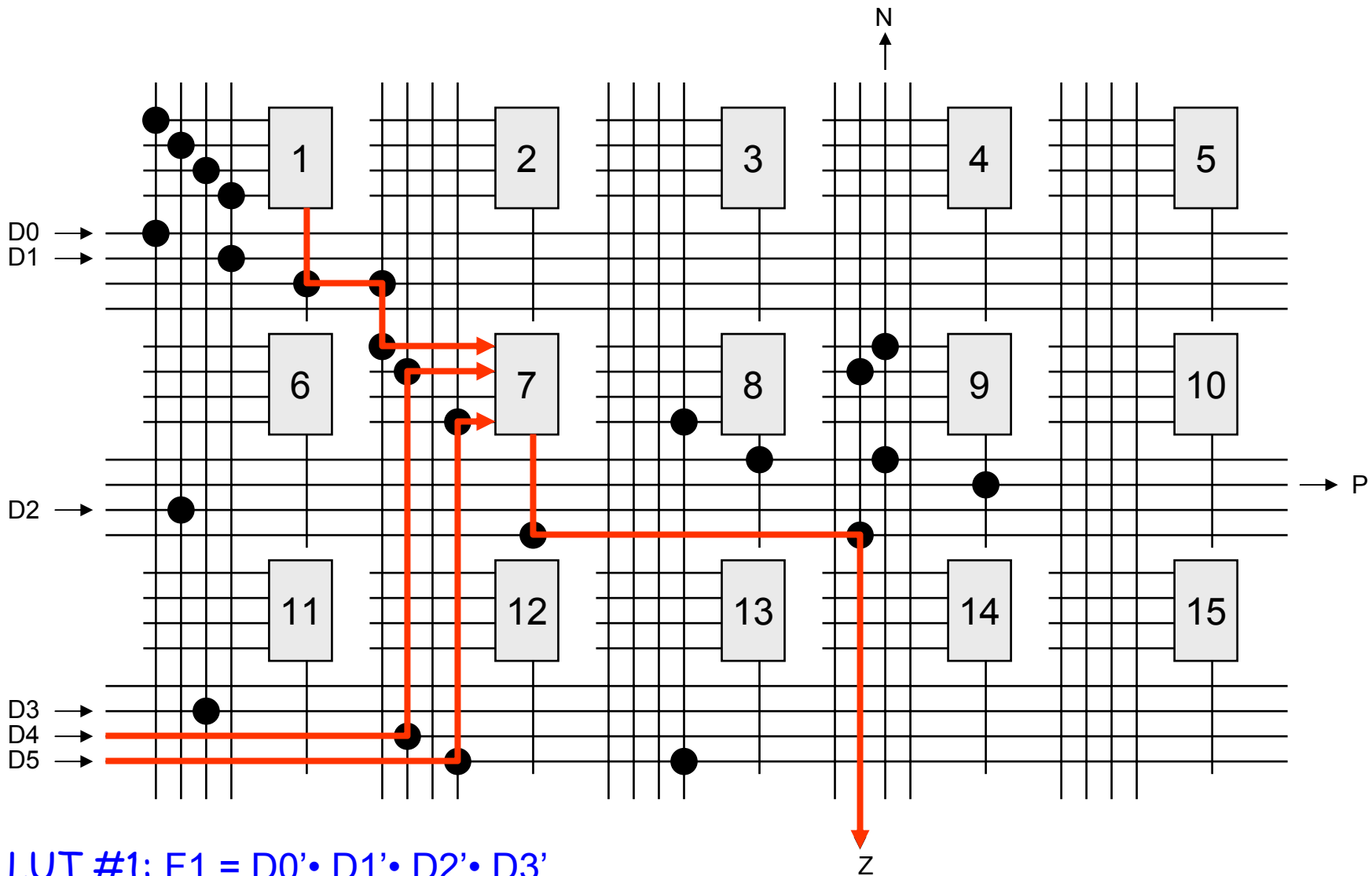LUT #9: $F4 = Z' \cdot N' \Leftrightarrow P$ output




LUT #1: $F1 = D0' \cdot D1' \cdot D2' \cdot D3'$

LUT #7: $F2 = F1 \cdot D4' \cdot D5' \Leftrightarrow Z$ output

LUT #8: $F3 = D5 \Leftrightarrow N$ output

 LUT #9: $F4 = Z' \cdot N' \Leftrightarrow P$ output




LUT #1: $F1 = D0' \cdot D1' \cdot D2' \cdot D3'$

LUT #7: $F2 = F1 \cdot D4' \cdot D5' \Leftrightarrow Z$ output

LUT #8: $F3 = D5 \Leftrightarrow N$ output

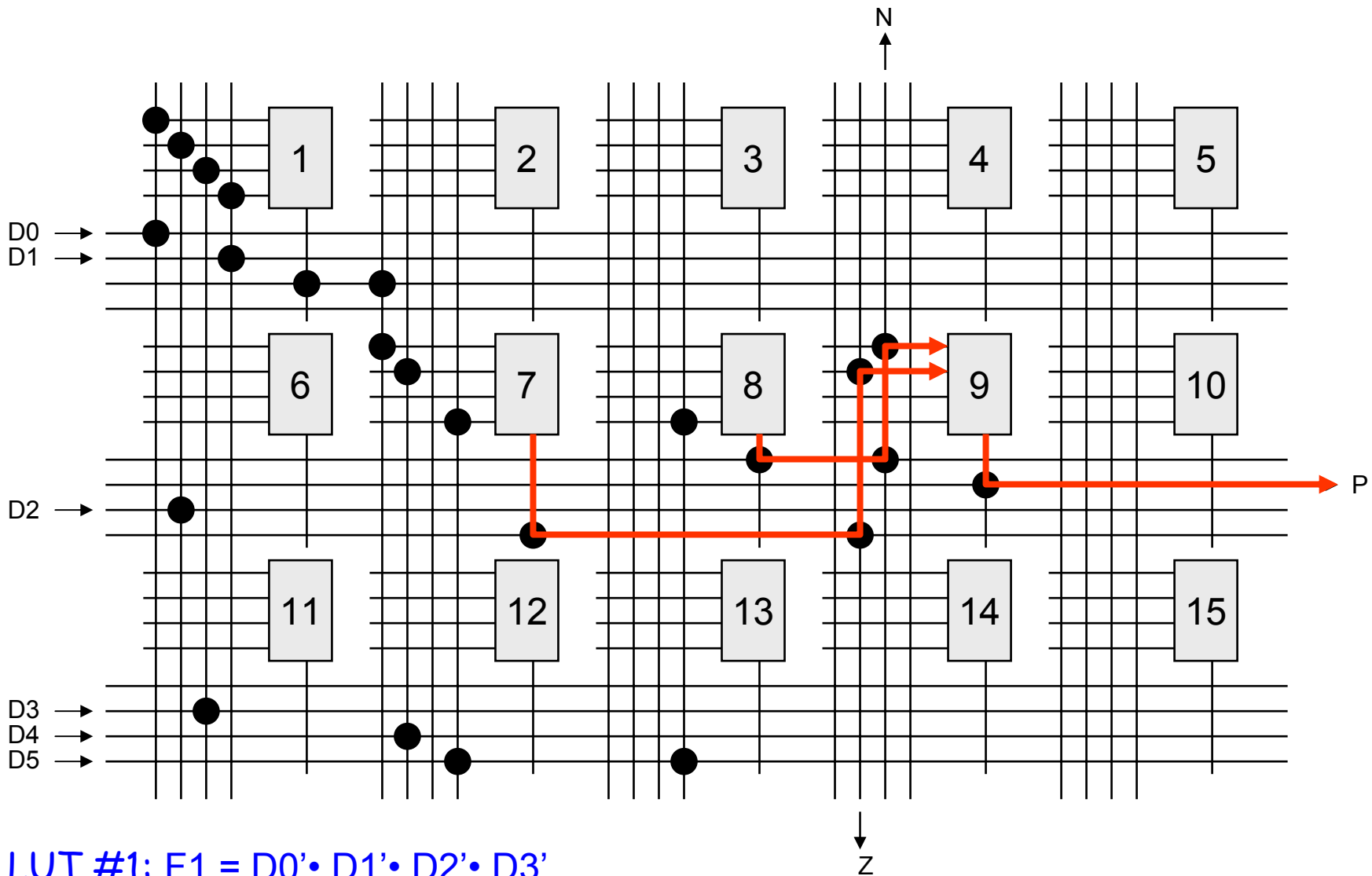LUT #9: $F4 = Z' \cdot N' \Leftrightarrow P$ output



LUT #1: $F1 = D0' \cdot D1' \cdot D2' \cdot D3'$

LUT #7: $F2 = F1 \cdot D4' \cdot D5' \Leftrightarrow Z$ output


LUT #8: $F3 = D5 \Leftrightarrow N$ output

LUT #9: $F4 = Z' \cdot N' \Leftrightarrow P$ output

Configuring an FPGA

- An FPGA contains a configuration pin
 - Configuration bits are shifted into FPGA using this pin, one bit per cycle
 - Configuration bits in FPGA linked into a long shift register (SIPO)
- Examples on following slides ⇔ *conceptual*
 - Commercial devices slightly different

Structure of a 3LUT

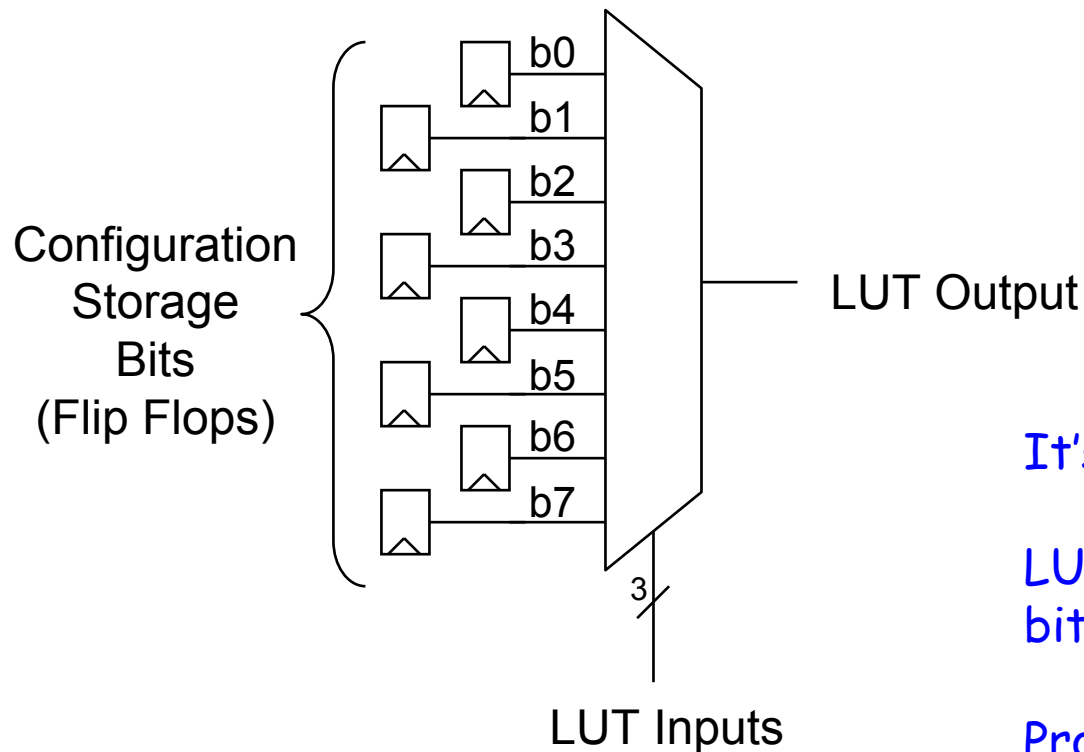


It's just an 8:1 MUX

LUT inputs select which config bit is sent to LUT output

Programming LUT function \Leftrightarrow setting configuration bits


How are the Configuration Bit Flip Flops Loaded?

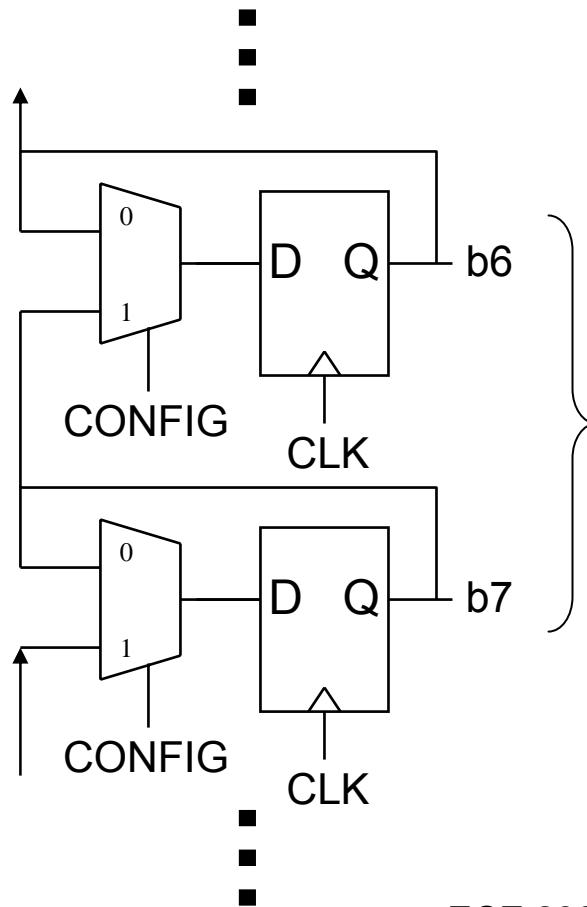A serial-in/parallel-out (SIPO) shift register



These are the configuration bits which the LUT selects from

 Configuring the Programmable Interconnect



Additional FPGA Features

Found in commercial FPGAs

Configurable Input/Output

- I/O buffers are at periphery of chip
 - Some will be inputs, some will be outputs
 - Set when chip configured
- Configurable I/O cell
 - Input static discharge protection
 - Input signal conditioning (voltage levels, ...)
 - Output drive
 - Fast, slow
 - Tri-state
 - Handles a variety of electrical standards
 - LVTTL
 - SGT
 - ...
- Configured at same time rest of chip is configured

Configuration Storage

- Actual configuration storage is *not* flip flops
 - Use SRAM memory cells
- Many chips can be *partially configured*
 - While rest of chip is running
- Different technologies
 - Program once
 - Fuse, anti-fuse configuration
 - Program multiple times
 - SRAM-based configuration

Programmable Interconnections

- Expensive to put programmable connections at *every* wire junction
 - Commercial parts \Leftrightarrow partially populate junctions
 - No or little loss of routing flexibility

Hierarchical Routing

- Collection of short, medium, and long wires
 - Both rows and columns
- Signals use wires that go distance needed
- CAD tools make determinations
- Like alleys, streets, expressways in a city
 - Longer distance ⇔ more limited access points

Clustered LE's

- Cluster: ≥ 1 LE
 - Example: clump of 4
 - Dedicated wires within groups of 4 LE's
- Closely related to hierarchical routing
- Higher performance
- Different vendors \Leftrightarrow different clustering

Embedded Function Units

- Place the following into the FPGA fabric:

multipliers

memories


I/O interfaces (*e.g.* gigabit serial links or ethernet PHY/MAC)

CPU's (PowerPC, ARM, ...)

- Result: higher speed, higher density designs

FPGAs Compared To Other Technologies

Performance vs. Flexibility

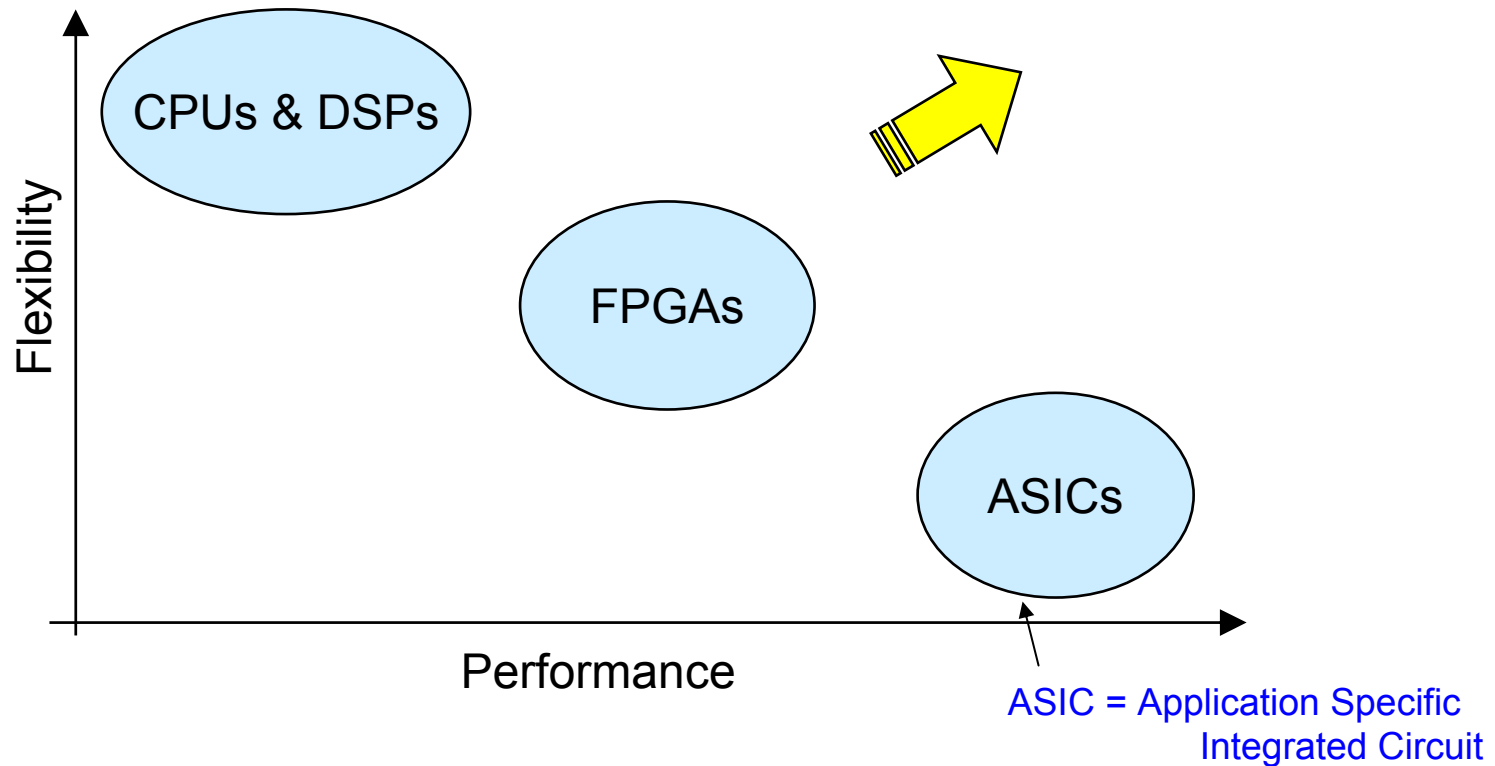

Goal: the performance of ASIC's with the flexibility of programmable processors.

FPGAs vs. CPUs - Flexibility

- Any function can be programmed to run on a CPU
 - Programming is relatively simple to do
- Any function can also be configured onto an FPGA
 - Design is significantly harder
 - It is digital logic design
- Both CPUs and FPGAs can be reprogrammed (reconfigured) in the field

- Advantage: CPUs

FPGAs vs. CPUs - Performance

- 10+ years of research \Leftrightarrow 10x-100x performance advantage for FPGAs
- Custom hardware \Leftrightarrow
 - No fetch-decode-memoryAccess overhead
 - Significant parallelism and pipelining
- Case in point: 1998 SONAR beamformer on an FPGA
 - BYU Configurable Computing Lab research
 - 2×10^9 FLOP/sec *sustained*
 - 10x-80x faster than comparable CPU technology
- Advantage: FPGAs

FPGAs vs. ASICs - Flexibility

- ASIC is a *static* hardware design
 - Wires and transistors fixed at manufacture time
 - Cannot be upgraded (reprogrammed) in the field
- FPGA can be configured (and reconfigured)
 - FPGA platform \Leftrightarrow used for a variety of applications
 - CCM = Custom Computing Machine (based on FPGAs)
- Advantage: FPGAs

FPGAs vs. ASICs - Performance

- Both ASICs and FPGAs are *custom* hardware designs
- FPGA *configurability* comes at a cost
 - FPGA density = 1/10th to 1/100th of an ASIC
- Result:
 - Higher cost chip for FPGA
 - Higher performance/silicon area for ASIC
 - For some/many applications:
 - FPGA just not fast/big enough
- Advantage: ASICs

FPGAs vs. ASICs - Cost

- Once the design is complete:
 - FPGAs can be programmed in seconds
 - Negligible up-front costs
 - No penalty for small volume
 - Per part cost very high
 - ASICs require time-consuming, expensive manufacturing process
 - Fabrication facility \geq \$1G
 - Significant up-front costs
 - Penalty for small volume
 - Per part cost very low
- Advantage: ??? (depends on volumes and application)

FPGA vs. ASIC Production Cost Example

- FPGA

- Non-recurring expenses (NRE) = \$0
- Per-part cost = \$20
(prices vary from a few \$'s to \$100's)
- Cost to produce 100 = \$2K
- Cost to produce 10^6 = \$20M

- ASIC

- NRE expenses = \$5M
- Per-part cost = \$1
- Cost to produce 100 = \$5M + \$100 \approx \$5M
- Cost to produce 10^6 = \$6M

Volume produced makes a big difference...

FPGAs vs. ASICs - Additional Points

- Manufacturing Time
 - FPGA = milliseconds for end customer
 - ASIC = weeks to months
- Fixing Bugs
 - FPGA = modify design + reconfigure FPGA
 - ASIC = modify design + remanufacture
- Advantage: FPGA

FPGAs vs. ASICs - Summary

- Two very different technologies
 - Flexibility: FPGA wins
 - Performance: ASIC wins
 - Risk: ?
 - Cost: ?
- Complex Decision
 - Only partially based on technical issues
 - Significant business issues
 - Risk
 - Time-to-market
 - Market characteristics (elasticity, price sensitivity, ...)

Design for FPGAs

1. Draw schematics or write HDL
2. CAD tool \Leftrightarrow maps to LUTs + FFs
3. CAD tool generates bitstream
4. Load bitstream \Leftrightarrow *configure* the FPGA

Design for ASICs

1. Draw schematics or write HDL
 2. CAD tool \Leftrightarrow map to physical silicon layout
 3. Send layout data to silicon *fab*
 4. Finished chip does intended function
-
- Step 1 fairly similar for FPGAs and ASICs
 - Major differences in later steps

FPGA/ASIC Vital Statistics

- A typical UG lab FPGA has:
 - 5,000-10,000 LUTs
 - 200-300 input/output buffers
 - Clock at ≈ 50 MHz

- A large modern CPU (Pentium circa 2004) has:
 - 125 million transistors
 - > 1000 input/output buffers
 - Clock at > 3 GHz

For More Information

- FPGA companies' WWW sites tend to have lots of information
 - Catering to a wide range of customers
 - Novice to expert
 - Low volume to high volume
 - Data sheets
 - Application notes
 - Success stories
 - CAD tools